

UNIVERSITY OF CALIFORNIA AT BERKELEY  
COLLEGE OF ENGINEERING  
DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCE

## EECS 141: Digital Integrated Circuits - Spring 2006

### Report Cover Sheet

#### TERM PROJECT: SRAM Design Cover Sheet

**Report 1 – Memory cell design**

Due Monday, March 20, 2006 by 10am in drop box.

Names
<b>Bill Hung</b>
<b>Chih-Chieh (Dennis) Wang</b>

Parameter	Pre-design estimate	Units
<i>Cell area</i>	13.3632 (928 $\lambda^2$ )	$\mu\text{m}^2$
<i>Read noise margin</i>	250	mV
<i>Voltage rise during read</i>	393.6	mV

	GRADE
Approach, result and correctness (60%)	
Report (40%)	
TOTAL	

# Table of Content

TERM PROJECT: SRAM Design Cover Sheet .....	1
Table of Figures .....	2
PHRASE I Minimize a SRAM Cell .....	5
Sizing Methodology .....	5
Pull Up Transistors .....	5
Access Transistors .....	5
Pull Down Transistors .....	6
Read Operation .....	7
Write Operation .....	7
HSPICE Stimulation .....	7
Cadence Layout .....	8
Phase I Summary .....	8
Glossary .....	9
Static Noise Margin HSPICE with Pulldown Transistor Width of $1.2 \times 0.36$ .....	1
Read Margin HSPICE Simulation .....	3
Transient Analysis with switch .....	7

# Table of Figures

Figure 1 High Level SRAM array block diagram .....	4
Figure 2 SRAM Schematic .....	5
Figure 3 Read margin and Write margin with $W_1 = 0.432\mu\text{m}$ . Read Margin is 450mV, which is larger than the required 400mV. ....	7
Figure 4 Static Noise Margin VTC HSPICE Plot .....	1
Figure 5 Read margin VTC .....	3
Figure 6 Write 0 to q followed by a read .....	5

# SRAM Cell Design

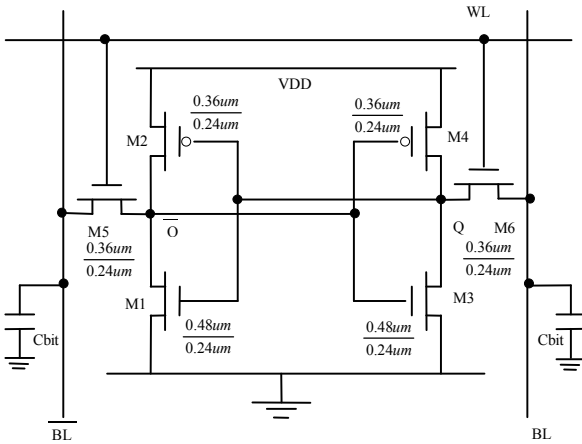


Figure 1: SRAM Cell Schematic

 


Figure 2: Cadence SRAM Cell Layout

(left) The pull-up transistors and the access transistors are minimum sized ( $W/L=0.36/0.24$ ) to give a pull-up ratio of  $1(<1.5)$ . The pull-down transistors are sized  $W/L=0.48/0.24$  to meet the  $0.4V$  read margin. The cell ratio is  $1.33(>1.2)$ . (right) The goal of the layout is to make it work with minimum size.

 


Figure 3: HSPICE Static Noise Margin

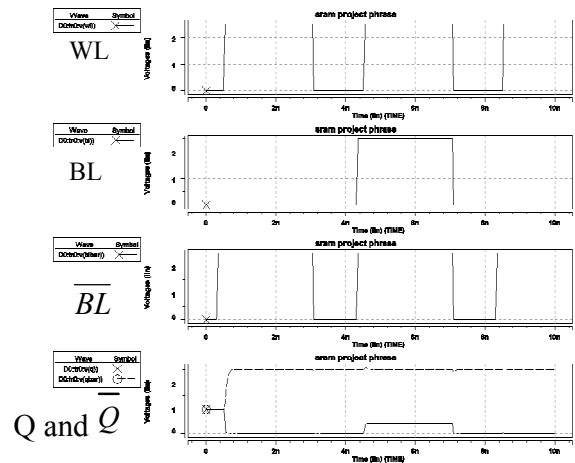


Figure 4: HSPICE Read and Write Simulation

(left) Voltage Transfer Curve (VTC) of an inverter and a half cell taken from the SRAM cell. The read margin of  $0.4V$  is met. Note that the two axes are in different scale. (right) A write simulation wrote a zero into the SRAM cell, followed by a read simulation shows the read margin is below  $0.4V$ . Note that when the word line is low initially,  $Q$  and  $\bar{Q}$  have don't care values

 


Figure 1 High Level SRAM array block diagram



the SRAM design. Larger L can give less leakage because of longer channel length, but it adds more load to the bit line. In this design, the L of the access transistors are at their minimum lengths. In order to compensate for the minimum lengths of the access transistors, the width (W) of the pull down transistors are increased.

### **Pull Down Transistors**

The width of the pull down transistors (M1 and M3) is the main parameter to optimize. The goal of the minimizing is to make sure “the SRAM still works” as expected. The critical point to meet the specification to have  $\Delta V$  of  $\bar{Q}$  below 0.4V. That is :

$\Delta V(\bar{Q}) < 0.4V$  . According to the equation

$$CR = \frac{W_1 / L_1}{W_5 / L_5} \quad \text{Equation 2:Cell Ratio [Rabaey, 659]}$$

where CR is called the cell ratio [Rabaey, 659]

CR is about 1.2[Rabaey, 659]. So

$$CR = \frac{W_1 / L_1}{W_5 / L_5} = \frac{W_1}{W_5} = 1.2$$

$$W_1 = 1.2 \cdot W_5$$

If  $W_5$  is minimum sized,  $W_1$  is 1.2 times the minimum size. As HW3#3a suggested, the minimum NMOS has  $L=0.24\mu\text{m}$ , and  $W=0.36\mu\text{m}$ . So,

$$W_1 = 1.2 \cdot (0.36\mu\text{m}) = 0.432\mu\text{m}$$

However, with  $W_1 = 0.432\mu\text{m}$ , the read margin exceed the 0.4V specification.

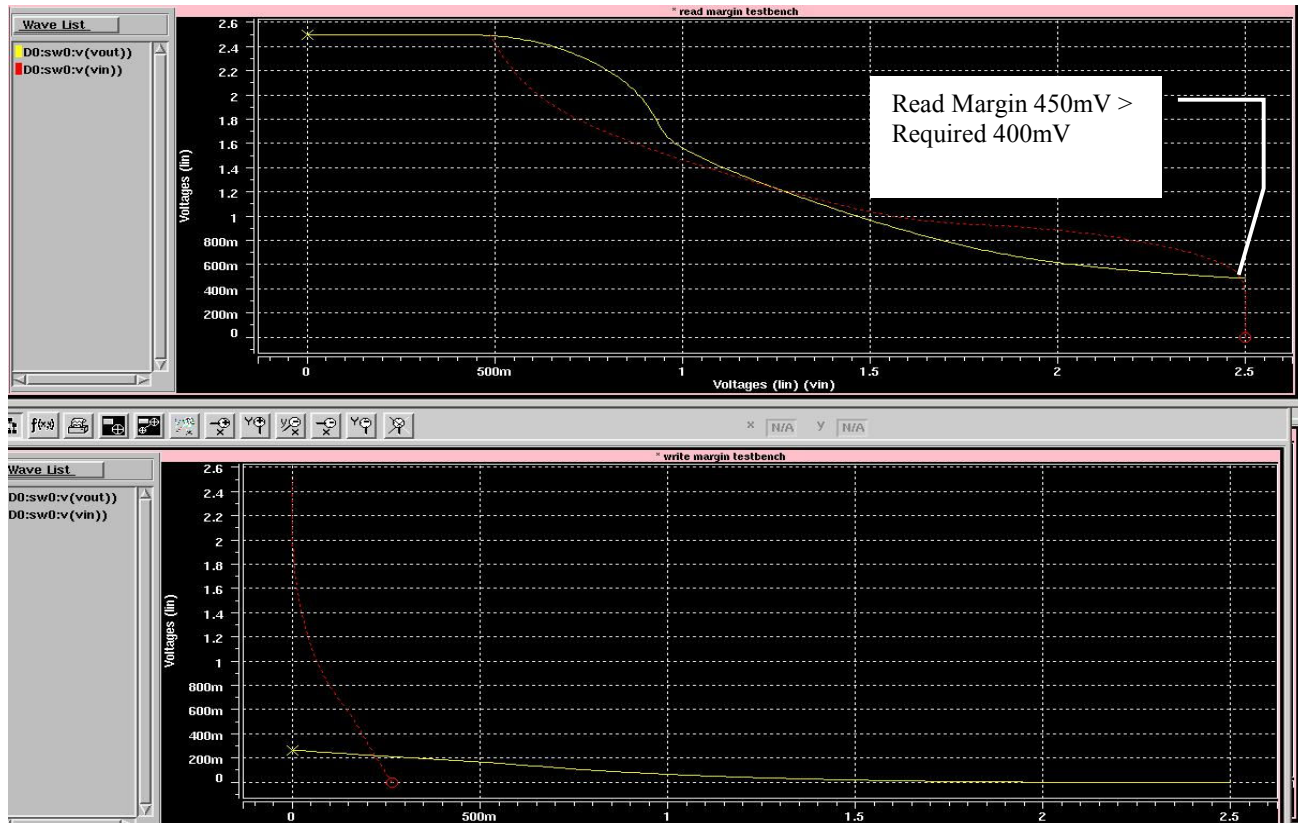


Figure 3 Read margin and Write margin with  $W_1 = 0.432\mu\text{m}$ . Read Margin is 450mV, which is larger than the required 400mV.

Therefore, we increased the width to  $0.48\mu\text{m}$ ,  $CR = 1.33$ , which will give a read margin of 0.3936V. A read margin of 0.3936V is better than the required read margin 0.4V. Also note that the width needs to be a multiple of  $\lambda$  in the layout,  $0.12\mu\text{m}$ . At this point, both read margin and write margin are below 0.4V. Note that we could increase the width even further to lower the read margin, but since our goal is to minimize the size, we used  $0.48\mu\text{m}$ .

## Read Operation

The read margin has to be met. The read margin is designed so that  $\bar{Q}$  does not exceed 0.4V during a read operation.


## Write Operation

This project needs to meet the write margin. According to Professor Nikolic, the write margin is “the highest voltage on  $BL/\overline{BL}$  that writes a zero into the cell”.

## HSPICE Stimulation

As we increase the width of the pulldown nmos transistors, the read margin decreases.

## Cadence Layout

 

## Phase I Summary

Horizontal Length = 7.2um

Vertical Height = 2.16um

Area =  $15.552 \text{ um}^2 = 1080\lambda^2$

Hours = 39 hours



## Glossary

### Area

The smallest rectangle enclosing the repetitive pattern. In this case, from a contact of one side to the contact of another side.

### Read Margin

is designed so that  $\overline{Q}$  does not exceed 0.4V during a read operation.

### SRAM

Static Random Access Memory

### Write Margin

is “the highest voltage on  $BL/\overline{BL}$  that writes a zero into the cell

# Static Noise Margin HSPICE with Pulldown Transistor Width of 1.2\*0.36

 


Figure 4 Static Noise Margin VTC HSPICE Plot

## Static Noise Margin

```
.lib '/home/ff/ee141/MODELS/g25.mod' TT

*****
* Parameter
*****
.param vddp=2.5
.param wpulldown=0.36u*1.2
.param pmoswidth=0.36u

*****
* Netlist
*****
VDD vdd 0 'vddp'
vq q 0 2.5V

*M<name> <drain> <gate> <source> <bulk> <model> <geometry>

M1 qbar q 0 0      nmos l=0.24u w='wpulldown'
M2 qbar q vdd vdd  pmos l=0.24u w='pmoswidth'

*****
* Analysis
*****
*nomod= no model info from library
.options post=2 nomod

*.op makes hspice determines DC operating point
.op

.dc vq 0 2.5 0.01

.end
```

# Read Margin HSPICE Simulation

 


Figure 5 Read margin VTC

```
** inverter subcircuit
.subckt my_inv vin vout vdd vss
.param wpulldown='0.48u'
.param pmoswidth=0.36u
M1 vout vin vss vss nmos l=0.24u w='wpulldown'
M2 vout vin vdd vdd pmos l=0.24u w='pmoswidth'
.ends
```

```
* read margin testbench
.lib '/home/ff/ee141/MODELS/g25.mod' TT
.inc 'circuit.sp'
Vdd vdd 0 2.5
Vin VIN 0 dc 2.5
xinv Vin Vout vdd 0 my_inv
M5 vblbar vdd Vout 0 nmos l=0.24u w=0.36u
Vblbar vblbar 0 2.5
.dc Vin 0 2.5 0.01
.option post
.END
```

```
$DATA1 SOURCE='HSPICE' VERSION='V-2004.03'
.TITLE 'sram project phrase'
q_max_rd      q_max_wr      temper      alter#
1.886e-02      0.3936      25.0000      1.0000
```

```
* Write margin testbench (not required for the report)
.lib '/home/ff/ee141/MODELS/g25.mod' TT
.inc 'circuit.sp'
Vdd vdd 0 2.5
Vin VIN 0 dc 2.5
xinv Vin Vout vdd 0 my_inv
M6 vbl vdd Vout 0 nmos l=0.24u w=0.36u
Vbl vbl 0 0
.dc Vin 0 2.5 0.01
.option post
.END
```

 


Figure 6 Write 0 to q followed by a read

SRAM PROJECT PHRASE

```
.lib '/home/ff/ee141/MODELS/g25.mod' TT

*****
* Parameter
*****
.param vddp=2.5
.param vwl=2.5
.param vbl=0
.param vblbar=0
* find the optimal nmos width
.param w = 1.32
.param wpulldown='0.48u'
.param pmoswidth=0.36u
* increase the size of capacitance
.param cright=.5pF
.param cleft=.5pF

*****
* Netlist
*****
*M<name> <drain> <gate> <source> <bulk> <model> <geometry>
M1 qbar q 0 0      nmos l=0.24u w='wpulldown'
M2 qbar q vdd vdd  pmos l=0.24u w='pmoswidth'
M3 q qbar 0 0      nmos l=0.24u w='wpulldown'
M4 q qbar vdd vdd  pmos l=0.24u w='pmoswidth'
M5 qbar wl blbar 0 nmos l=0.24u w=0.36u
M6 q wl bl 0       nmos l=0.24u w=0.36u

VDD vdd 0 'vddp'
*VWL wl 0 'vwl'

* generate pulses for word line and bit lines. In the first cycle, write
* a zero to q; in the second cycle, read 0 from q
VWL wl 0 pulse(0 2.5 .5n 0.05n 0.05n 2.5n 4n)
VBLBAR blbar 0 pulse(0 2.5 .3n 0.05n 0.05n 2.7n 4n)
VBL bl 0 pulse(0 2.5 4.3n 0.05n 0.05n 2.7n 8n)

Cblbar blbar 0 'cleft'
Cbl bl 0 'cright'

*****
* Analysis
*****
.options post=2 nomod
.op

.tran 0.01ns 10ns *sweep w 1.08 1.8 .06
* In both scenarios, we want to check the maximum voltage at q
.meas q_max_wr max v(q) from=.6n to=3.5n
.meas q_max_rd max v(q) from=4.6n to=7.5n

.END
```

## Transient Analysis with switch

SRAM PROJECT PHRASE

```
.lib '/home/ff/ee141/MODELS/g25.mod' TT

*****
* Parameter
*****
.param vddp=2.5
.param vwl=2.5
.param vbl=0
.param vblbar=0
* find the optimal nmos width
.param w = 1.32
.param wpulldown='0.48u'
.param pmoswidth='0.36u'
* increase the size of capacitance
.param cright='.5pF'
.param cleft='.5pF'

*****
* Netlist
*****
*M<name> <drain> <gate> <source> <bulk> <model> <geometry>
M1 qbar q 0 0 nmos l=0.24u w='wpulldown'
M2 qbar q vdd vdd pmos l=0.24u w='pmoswidth'
M3 q qbar 0 0 nmos l=0.24u w='wpulldown'
M4 q qbar vdd vdd pmos l=0.24u w='pmoswidth'
M5 qbar wl blbar 0 nmos l=0.24u w=0.36u
M6 q wl vx 0 nmos l=0.24u w=0.36u

* syntax for ideal switch: G1 node1 node2 VCR PWL(1) node3 V Resistance
* V Resistance, where node3 is the controlling voltage. For example, the
* syntax below said that the switch is controlled by phi1; if it is 0V,
* the off resistance is 100Gohm; if it is 2.5V, the on resistance is 1uohm
G1 vx bl VCR PWL(1) phi1 0 0,100G 2.5,1u
*G2 vx 0 VCR PWL(1) phi1 0 0,100G 2.5,1u
* controlling voltage source
Vphi1 phi1 0 pwl(0 0 .4n 0 0.4000001n 2.5 4.4n 2.5 4.4000001n 0 )

VDD vdd 0 'vddp'
*VWL wl 0 'vwl'

* generate pulses for word line and bit lines. In the first cycle, write
* a zero to q; in the second cycle, read 0 from q
VWL wl 0 pulse(0 2.5 .5n 0.05n 0.05n 2.5n 4n)
VBLBAR blbar 0 pulse(0 2.5 .3n 0.05n 0.05n 2.7n 4n)
VBL bl 0 pulse(0 2.5 4.3n 0.05n 0.05n 2.7n 8n)

Cblbar blbar 0 'cleft'
Cbl bl 0 'cright'

*****
* Analysis
*****
.options post=2 nomod
.op

.tran 0.01ns 10ns *sweep w 1.08 1.8 .06
* In both scenarios, we want to check the maximum voltage at q
.meas q_max_wr max v(q) from=.6n to=3.5n
.meas q_max_rd max v(q) from=4.6n to=7.5n

.END
```